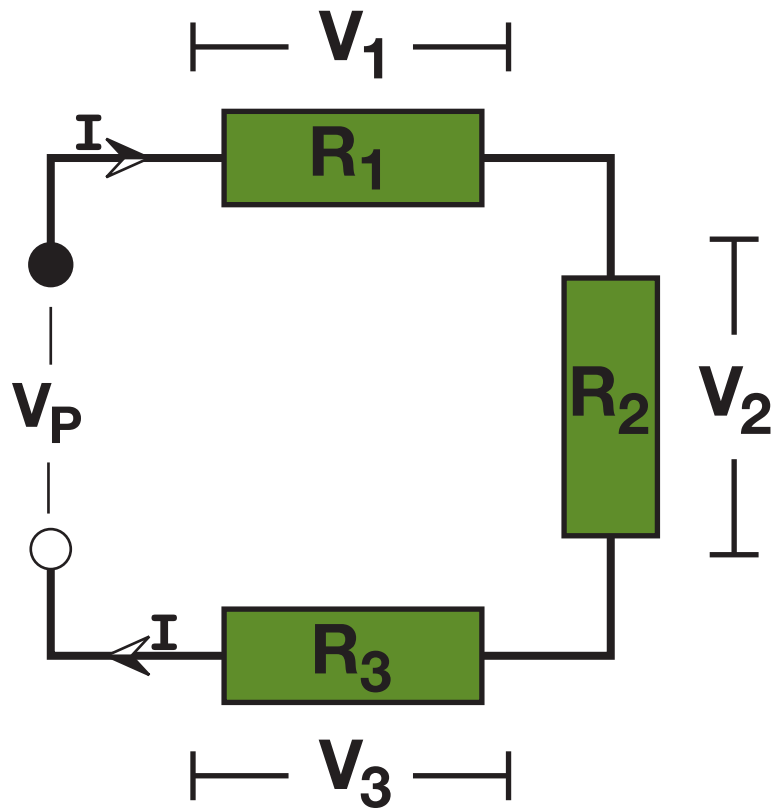


$$V_P = \begin{array}{|l} \text{Total Voltage} \\ \text{Applied by} \\ \text{Power Supply} \end{array}$$


$$R_t = \begin{array}{|l} \text{Total} \\ \text{Circuit} \\ \text{Resistance} \end{array}$$

$$I_t = \begin{array}{|l} \text{Total} \\ \text{Circuit} \\ \text{Current} \end{array}$$

Series Circuit




Parallel Circuit

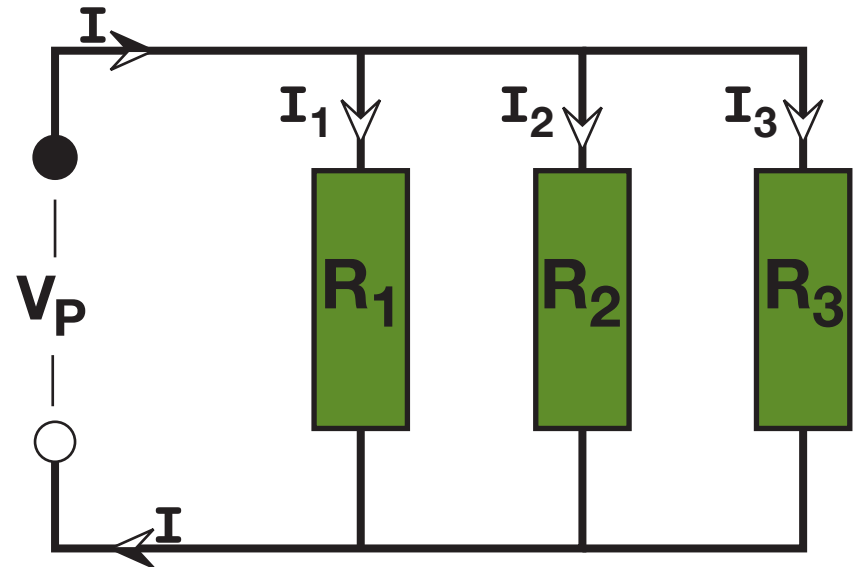

$$V_P = \text{Total Voltage Applied by Power Supply}$$

$$R_t = \text{Total Circuit Resistance}$$
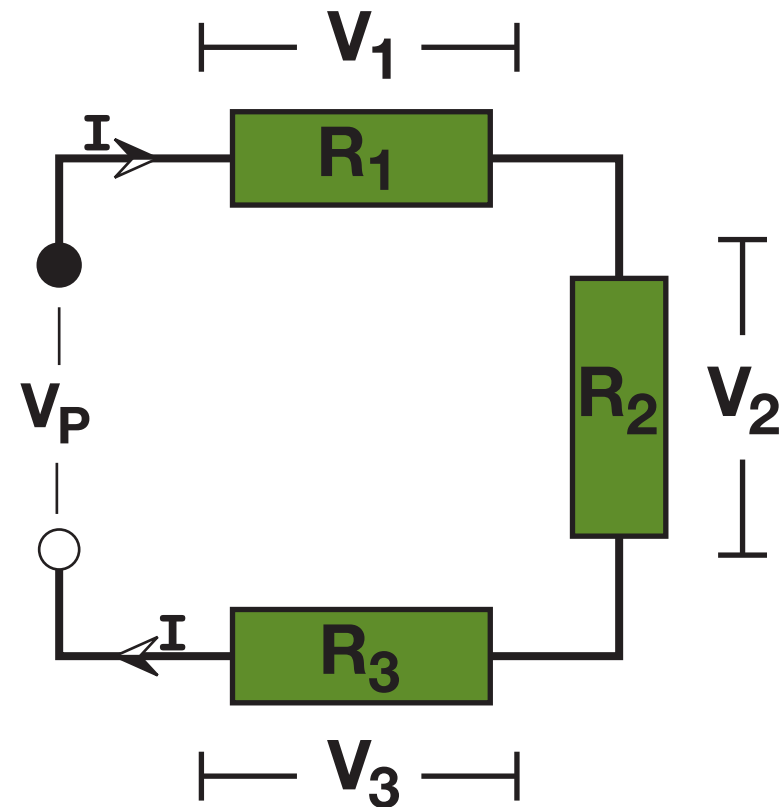
$$I_{\rightarrow} = \text{Total Circuit Current}$$



$$I_{\rightarrow} = \text{Common Current}$$

The current through each individual component is the same as the total circuit's current which is a function of the total voltage and total resistance

$$= \frac{V_P}{R_t}$$

$$V_P = -OR- V_1 + V_2 + V_3$$


$$(I_{\rightarrow} * R_1) + (I_{\rightarrow} * R_2) + (I_{\rightarrow} * R_2)$$

$$R_t = R_1 + R_2 + R_3$$

$$V_P = \boxed{\text{Total Voltage Applied by Power Supply}}$$

$$R_t = \boxed{\text{Total Circuit Resistance}}$$
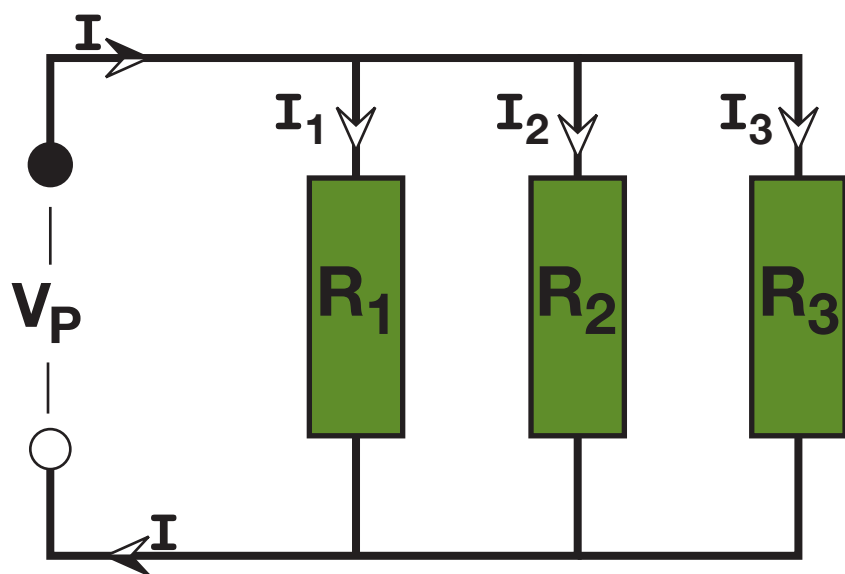
$$I_{\rightarrow} = \boxed{\text{Total Circuit Current}}$$



$$V_P = \text{Common Voltage}$$

The total circuit voltage remains constant among each individual component within the circuit

$$= I_{\rightarrow} * R_t$$

$$I_1 + I_2 + I_3$$

$$I_{\rightarrow} = -OR-$$

$$\left(\frac{V_P}{R_1} \right) + \left(\frac{V_P}{R_2} \right) + \left(\frac{V_P}{R_3} \right)$$

$$R_t = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$